

Roll: EE22B056

Name: Piyush Gupta

Assignment 1

Design of a 90° Hybrid Coupler

Scattering Matrix at Design Frequency

0.0036	0.697	0.704	0.0082
0.697	0.0036	0.0082	0.704
0.704	0.0082	0.0036	0.697
0.0082	0.704	0.697	0.0036

Summary

Design Frequency: 22 GHz

Insertion Loss: 3.135dB



Coupling: 3.048dB

Isolation: 41.72dB

Directivity: 38.67dB

Bandwidth: 11GHz

Design/Simulation Schematics

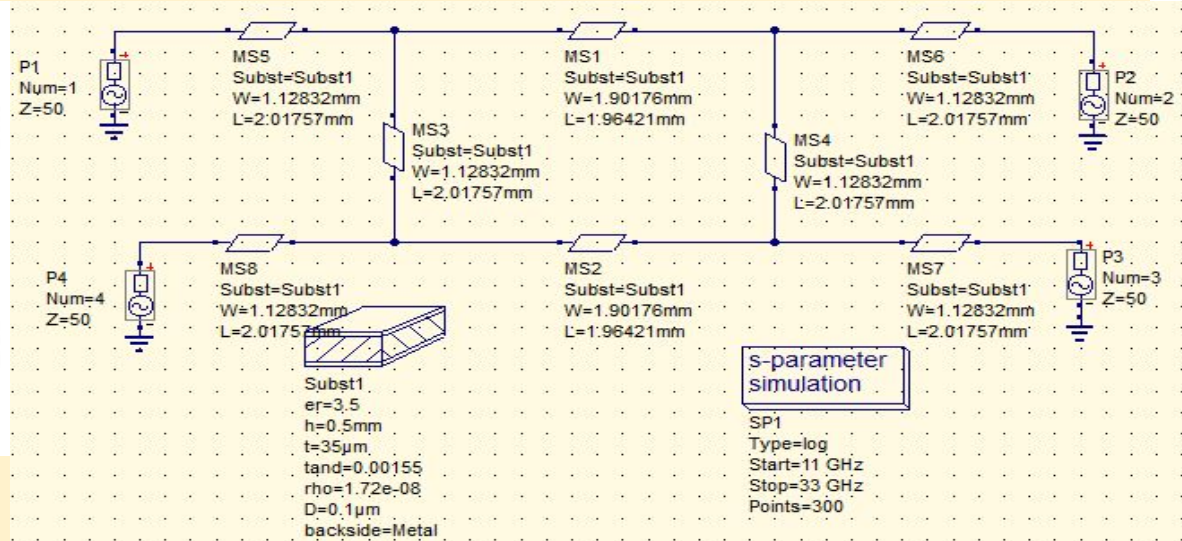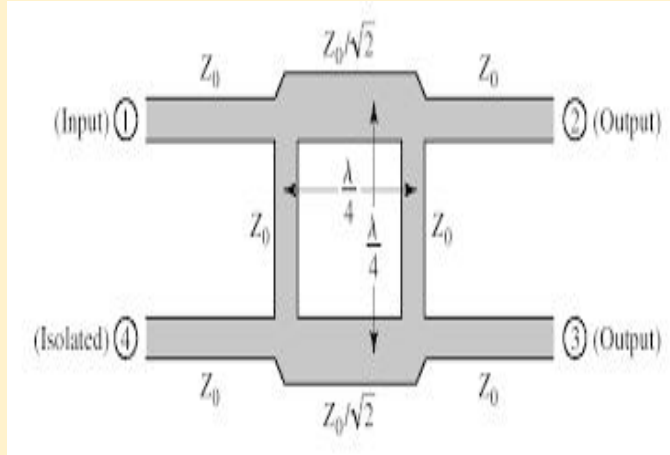

Comments/Remarks

To design this, the standard substrate RF-35 is chosen. From the data Sheet given,

Dielectric Constant=3.50

Loss Tangent=0.000155 @22Ghz


Thickness of dielectric(h)=0.5 mm

Thickness of c(t)=35 um

$S_{11}, S_{21}, S_{31}, S_{41}$ Magnitude Plot in dB


$S_{11}, S_{21}, S_{31}, S_{41}$ Phase Plot in Degree

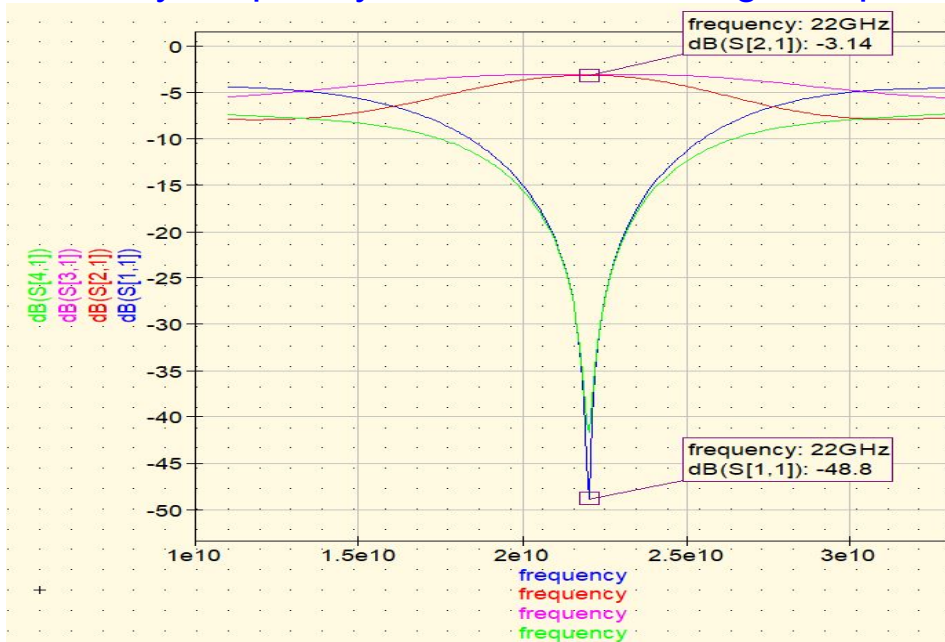As my frequency is 22GHz ,the design frequency range should be from 11GHz to 33GHz.



Comments/Remarks

We obtain nearly perfect power division of 3.14dB at port 2 and 3, and perfect isolation and return loss at port 4 and 1, respectively, at the design frequency 22GHz. All these quantities, however, degrade quickly as the frequency departs 22GHz.

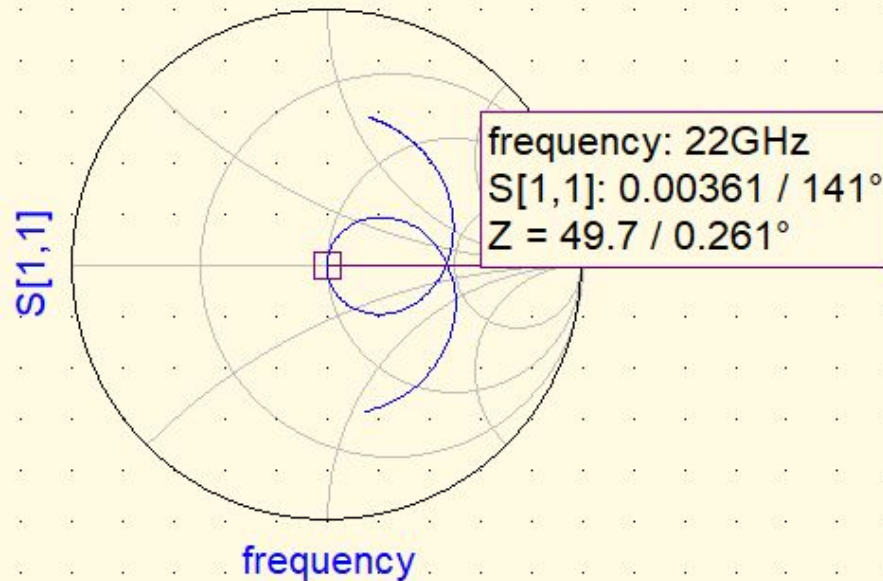S_{11} Plot in Smith-Chart

Put a marker on the S_{11} trace and find out the input impedance at your design frequency.

Each point on smith chart represents a unique impedance normalised to the characteristic impedance Z_0 of transmission line. After locating the point on smith chart which corresponds to S_{11} , we read the input impedance directly from the chart, we get $Z_{in} = 49.7 / 0.261$ ohms. The input impedance characterizes how a device interacts with the signals applied at its input port

Comments/Remarks

As Z_{in} is approximately equal to Z_0 , we can say that the port is almost matched. As they are equal, even the reflection coefficient will be Zero

S parameter in tabular format

0.00361 / 141°	0.697 / 89.5°	0.704 / -0.472°	0.00826 / 105°
0.697 / 89.5°	0.00361 / 141°	0.00826 / 105°	0.704 / -0.472°
0.704 / -0.472°	0.00826 / 105°	0.00361 / 141°	0.697 / 89.5°
0.00826 / 105°	0.704 / -0.472°	0.697 / 89.5°	0.00361 / 141°

Comment on the matching of the circuit.

Commonly, a reflection Coefficient below 10dB (which corresponds to approximately 0.1 in magnitude) is considered well matched in many applications. Here $S_{11}=0.00361$ which is less than 0.1. So it is considered to be matched.

Decide the type of design based on the properties of the S-matrix.

As $S_{11}=S_{22}=S_{33}=S_{44}$ and $S_{21}=S_{12}, S_{23}=S_{32}$..etc so it is symmetric and reciprocal. And it also satisfies the lossless conditions so it is lossless and matched. Therefore our application is symmetric, reciprocal, matched and lossless. Such a device is often referred to as a Magic Hybrid

Conclusion/ Comments/ Remarks

Remarks: So, based on the $S_{11}=0.00361$ value, port 1 is almost perfectly matched.

Comments: The coupling, Isolation, Directivity values must satisfy the equation $I=C+D$, i.e., $(41.72=3.048+38.67\text{dB})$. Here, this equation is satisfied.

Conclusion: The design and simulation of the 90 degree hybrid coupler using QUCS Studio have yielded valuable insights into its performance characteristics and practical considerations. Through thorough evaluation of insertion loss, return loss, isolation, Directivity, and Coupling, we have demonstrated the effectiveness of the designed coupler in achieving the desired functionality.